



# Traffic Light Control System


Using Verilog (VIVADO SOFTWARE)

**Designed by Akash Sonowal**

**Duration of Project : May 2022 - June 2022.**
 
## Overview

Designed a Automated Traffic Light Control System for Highway Intersection using Viavdo Software . Generally It is Designed for controlling Traffic for four way intersection or for Junction of Two Roads. The Following Diagram Shows a Rough View of the Designed Traffic Control System.



STATE	WEST-EAST	NORTH-SOUTH	DELAY(SEC)
0	GREEN	RED	5
1	YELLOW	RED	1
2	RED	RED	1
3	RED	GREEN	5
4	RED	YELLOW	1
5	RED	RED	1

## Specifications

- 1) Considered Lights as Binary Code :

Green : 100

Red : 001

Yellow : 010

- 2) Consider two set of Traffic Lights :

Light\_A and Light\_B

- 3) Divided the Possibility of Crossing and Traffic Signal in 6 possible combinations :

S0 : Light\_A= 001 ; Light\_B=100.

S1 : Light\_A= 010 ; Light\_B=100.

S2 : Light\_A= 100 ; Light\_B=100.

S3 : Light\_A= 100 ; Light\_B=001.

S4 : Light\_A= 100 ; Light\_B=010.

S5 : Light\_A= 100 ; Light\_B=100.

## Verilog Code :

```
module traffic_lights(  
    input clk,  
    input rst_n,  
    output reg[2:0] light_A,  
    output reg[2:0] light_B  
  
);  
    reg [2:0] Green;  
    reg [2:0] Red ;  
    reg [2:0] Yellow;  
  
    localparam s0 = 6'b000001,  
        s1 = 6'b000010,  
        s2 = 6'b000100,  
        s3 = 6'b001000,  
        s4 = 6'b010000,  
        s5 = 6'b100000;  
  
    reg[7:0] curr_state;  
    reg[7:0] next_state;  
  
    reg [7:0] count;  
    reg [7:0] count_en;  
    reg count_done;  
  
    localparam SEC5 = 8'd50,    SEC1 = 8'd10;  
  
    always@(posedge clk or negedge rst_n) begin
```

```
if(!rst_n) begin
    count <= 8'b0;
    count_done <= 8'b0;

end

else begin
    Green =8'b100;
    Red =8'b001;
    Yellow =8'b010;
    case(count_en)
    2'b01:
        begin
            count_done <=0;
            if(count <SEC5 - 1)
                count <= count + 1'b1;
            else begin
                count <= 0;
                count_done <= 1;
            end
        end
    2'b10:
        begin
            count_done<=0;
            if(count <SEC1 - 1)
                count <=count + 1'b1;
            else begin
                count <= 0;
                count_done <= 1;
            end
        end
    default: begin
        count <= 0;
        count_done <=0;
    end
end
```

```
        end
    endcase
end
end

always@(posedge clk or negedge rst_n) begin
    if (!rst_n) begin

        curr_state <= s0;
    end
    else begin
        curr_state <= next_state;
    end
end

always @(*)
    case(curr_state)
    s0: begin
        count_en = 2'b01;
        if(count_done)
            next_state = s1;
        end
    s1: begin
        count_en = 2'b10;
        if(count_done)
            next_state = s2;
        end
    s2: begin
        count_en=2'b10;
        if(count_done)
            next_state = s3;
        end
    s3: begin
        count_en=2'b01;
```

```
        if(count_done)
            next_state = s4;
        end
s4: begin
    count_en=2'b10;
    if(count_done)
        next_state = s5;
    end
s5: begin
    count_en=2'b10;
    if(count_done)
        next_state = s0;
    end
default: begin
    next_state = s0;
    count_en =2'b00;
    end
endcase

always@(posedge clk or negedge rst_n) begin
    if (!rst_n) begin
        light_A = 3'b000;
        light_B = 3'b000;
    end
    else begin
        case (next_state)
            s0:begin
                light_A<=3'b001;
                light_B<=3'b100;
            end
            s1:begin
                light_A<=3'b010;
                light_B<=3'b100;
            end
        endcase
    end
end
```

```
s2:begin
    light_A<=3'b100;
    light_B<=3'b100;
end
s3:begin
    light_A<=3'b100;
    light_B<=3'b001;
end
s4:begin
    light_A<=3'b100;
    light_B <=3'b010;
end
s5:begin
    light_A <= 3'b100;
    light_B <= 3'b100;
end
default: begin
    light_A = 3'b000;
    light_B = 3'b000;
end
endcase
end
end
endmodule
```



# OUTPUT :



## OUTPUT :

